
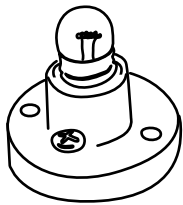


A simple circuit


What you need.

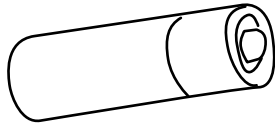


Bulb and holder



Battery

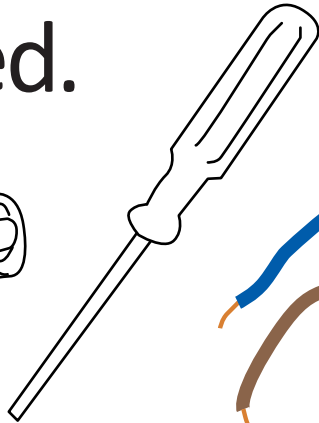

Screwdriver

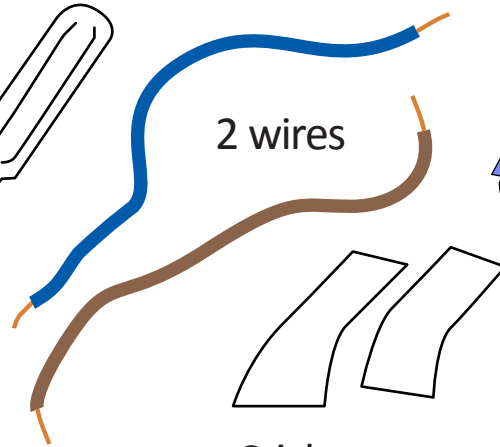

2 wires

Sticky tape

